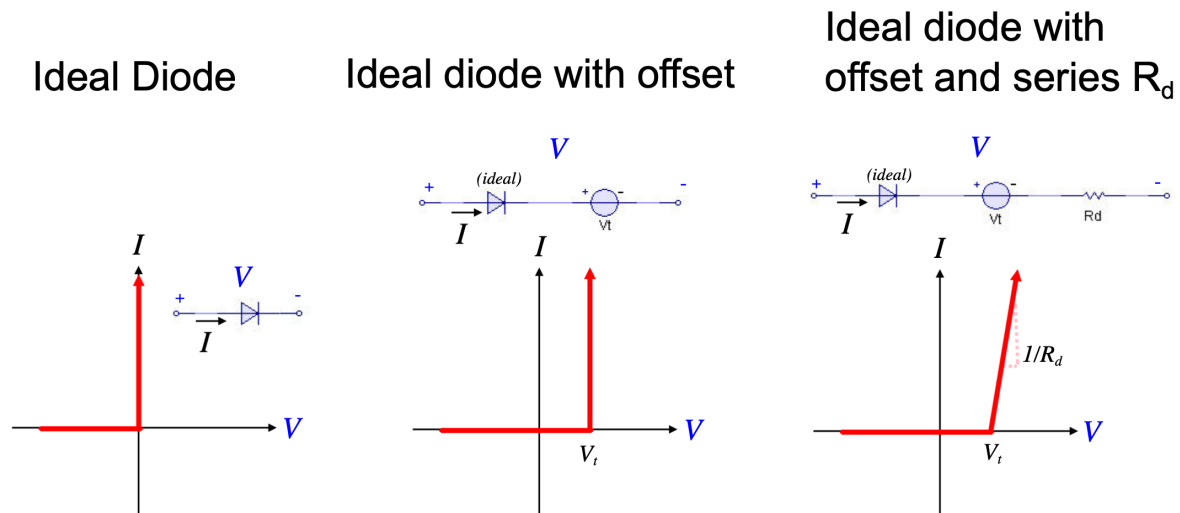


# Lab 11

Figure 1. Illustrations of I-V characteristics of different diode models.



CC BY-SA 2.5, <https://commons.wikimedia.org/w/index.php?curid=56267294>

Figure 2. Non-LED diodes used in this lab.


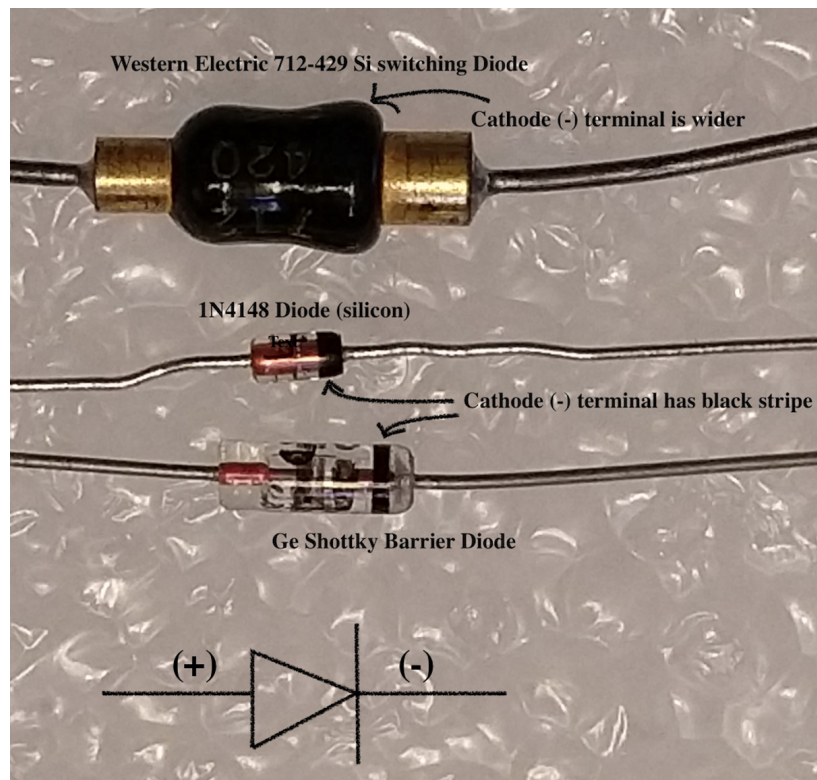


Figure 3. Circuit diagram.

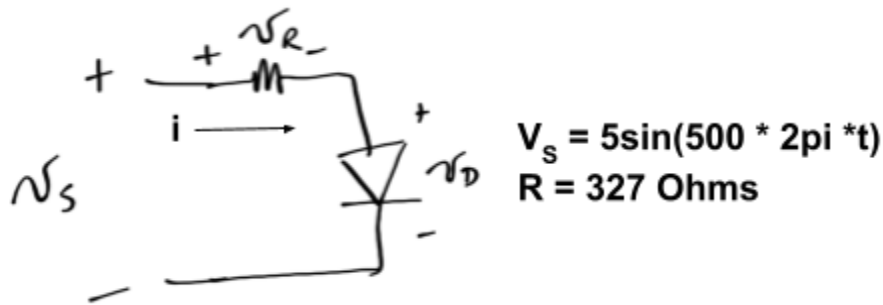

Channel 1 of Scopy's wave generator function was used to provide the source voltage  $V_s$ . A DMM was used to measure the resistance  $R$ . Scopy was used to measure  $V_R$  and  $V_D$  for the above circuit built with a number of different diodes. Channel 1 of the oscilloscope was connected across the resistor to measure  $V_R$ , while Channel 2 of the oscilloscope was connected across the diode to measure  $V_D$ . Each dataset was exported and loaded into Python.

Diodes used in this lab:

- White LED
- Red LED
- Blue LED
- Green LED
- Yellow LED
- Red leg of RGB diode
- Green leg of RGB diode
- Blue leg of RGB diode
- Western Electric 712-429 Si switching diode.
- 1N4148 Si diode
- AA-442 Ge Schottky diode


In Python, the current  $i$  was calculated using Ohm's Law and the measured resistance and  $V_R$  data.  $V_R = iR$ , so  $i = V_R/R$ . The calculated current for each dataset was then used to generate I-V curves for each diode.

Figure 4. Python code to calculate current.

```
# calculate current --> vr = i * R
r = 327 # Ohms


#i = vr / r
i_green = vr_green / r
i_g_rgb = vr_g_rgb / r
i_blue = vr_blue / r
i_b_rgb = vr_b_rgb / r
i_red = vr_red / r
i_r_rgb = vr_r_rgb / r
i_yellow = vr_yellow / r
i_white = vr_white / r
i_we = vr_we / r
i_ge = vr_ge / r
i_n = vr_n / r
```

Figure 5. I-V curves plotted with Python.

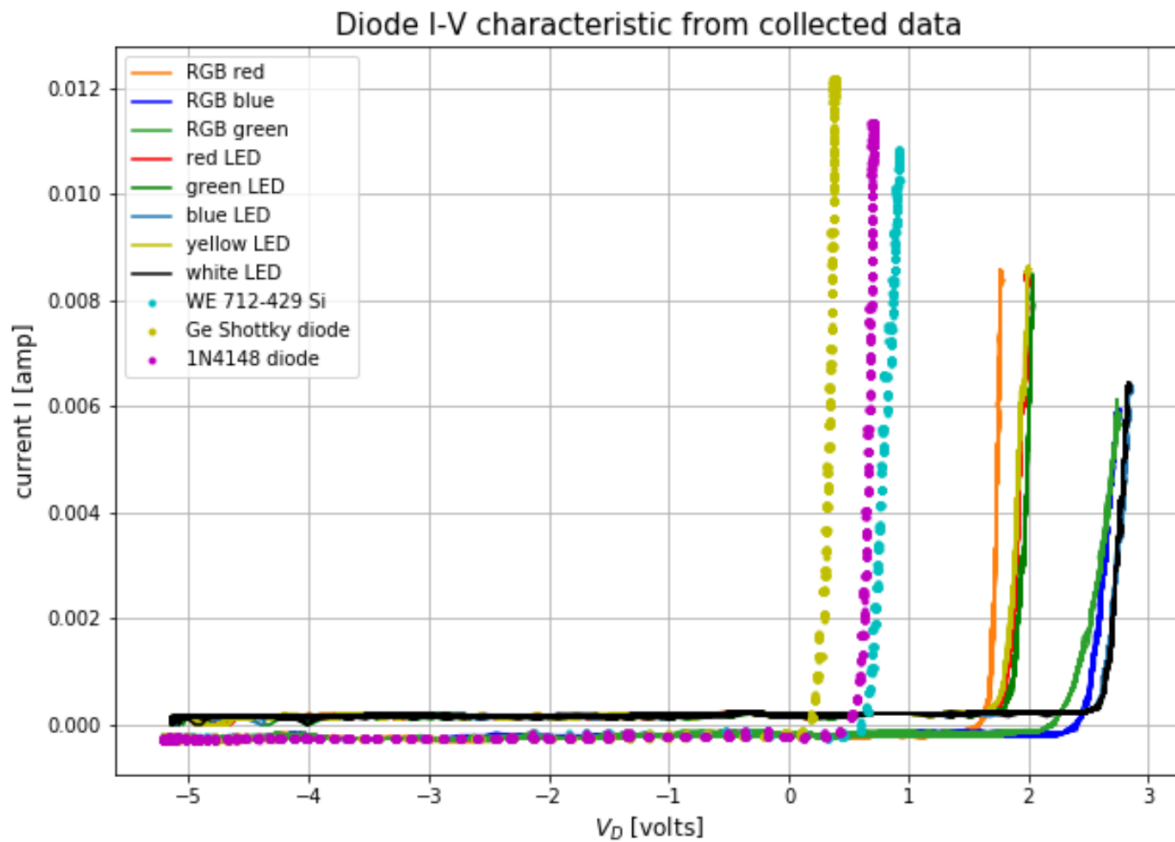

Plotting each diode's I-V curve on the same graph obscures some of the data, as several of the diodes display very similar behavior. Using limits on the x-axis, I separated the I-V curves into three separate plots to better see each individual I-V curve.

Figure 6. Separated I-V curves plotted with Python.

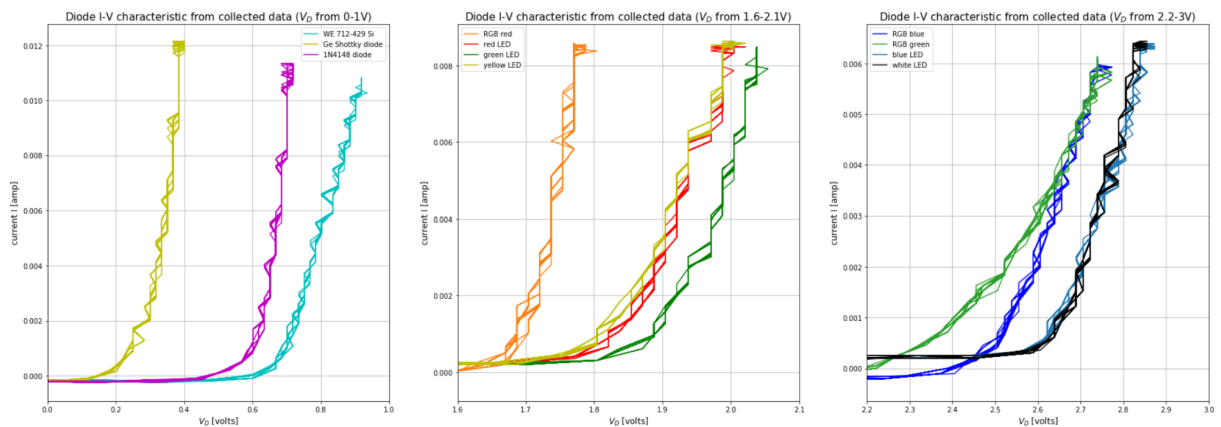

To estimate the values of  $V_t$  and  $R_d$  for each diode, I used a linear regression function in Python to fit a line of best fit to the portion of the I-V curve where current is greater than 0.002 Amps. This was chosen to avoid the “knee” region of the graph while still having sufficient data points.

By visual inspection of the plotted I-V curves, all of the diodes used seem to fit the model of an ideal diode with an offset and series resistance. From the given background information,  $V_t$  is the x-intercept of a line fit to the I-V curve and  $R_d$  is the inverse of that line's slope.

A Python method was written and used to determine the linear fit to any of the datasets. This fit was then used to calculate  $V_t$  and  $R_d$ .

*Figure 7. Method written in Python to determine the linear fit of an I-V curve at current > 0.002A.*

```
def findFit(vd, i):
    lin_i_indices = np.asarray(np.where(i > 0.002))
    num_pts = lin_i_indices.size
    lin_vd = np.zeros(num_pts)
    lin_i = np.zeros(num_pts)

    for j in range(num_pts):
        current_index = lin_i_indices[0,j]
        lin_vd[j] = vd[current_index]
        lin_i[j] = i[current_index]

    slope, intercept, r_value, p_value, std_err = stats.linregress(lin_vd, lin_i)
    line = (slope * lin_vd) + intercept

    return line, lin_vd, slope, intercept
```

Using the fit-finding method,  $V_t$  and  $R_d$  were calculated for each diode. To check the fit, the calculated line and  $V_t$  values were plotted with the original data and inspected visually.

*Figure 8. Example calculation of fit line,  $V_t$ , and  $R_d$  for the blue leg of the RGB diode.*

```
# linear fit to region where current > 0.002amp
fit_b_rgb = findFit(vd_b_rgb, i_b_rgb)
# vt = x-intercept of linear fit = (-y-intercept)/slope
vt_b_rgb = (-1*fit_b_rgb[3])/fit_b_rgb[2]
# Rd = 1 / slope
rd_b_rgb = 1 / fit_b_rgb[2]

print('RGB BLUE')
print('vt =', np.round(vt_b_rgb, 3), 'V')
print('Rd =', np.round(rd_b_rgb, 3), 'Ohms')
#print('\n')
```


```
RGB BLUE
vt = 2.519 V
Rd = 37.3 Ohms
```

Figure 9. Example plot of fit line,  $V_t$ , and I-V curve for the blue leg of the RGB diode.

```
plt.figure(figsize=(7,7))
plt.title('Diode I-V characteristics with linear fits ( $V_D$  from 2.2-3V)')
plt.xlabel(' $V_D$  [volts]', fontsize=12)
plt.xlim(2.2,3)
plt.ylabel('current I [amp]', fontsize=12)

plt.plot(vd_b_rgb,i_b_rgb,'b.', label='RGB blue')
plt.plot(fit_b_rgb[1],fit_b_rgb[0],'b-', label='RGB blue fit line')
plt.plot(vt_b_rgb, 0, 'b*', markersize=15,label='RGB blue  $V_t$ ')

plt.legend()
plt.grid()
```

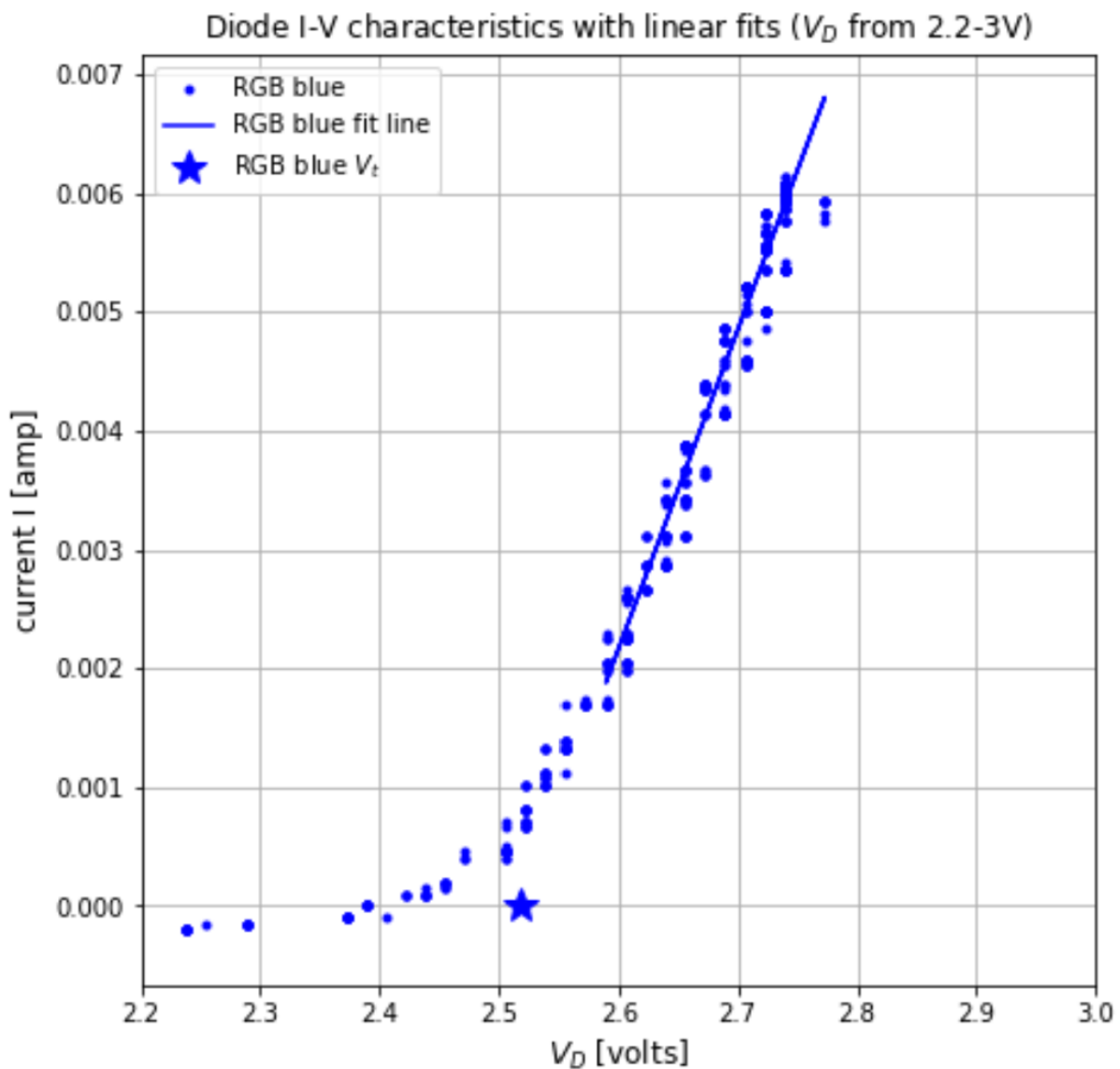

Looking at the graph, the spread of the data points around the line seems to be about 0.05V.

Figure 10. Table of calculated  $V_t$  and  $R_d$  values.

Diode	$V_t$ in volts	$V_t$ uncertainty	$R_d$ in Ohms
RGB blue leg	2.519	$\pm 0.05V$	37.3
RGB green leg	2.442	$\pm 0.05V$	51.043
Blue LED	2.628	$\pm 0.05V$	36.173
White LED	2.643	$\pm 0.05V$	30.807
RGB red leg	1.696	$\pm 0.05V$	9.522
Green LED	1.904	$\pm 0.05V$	16.606
Red LED	1.837	$\pm 0.05V$	19.631
Yellow LED	1.82	$\pm 0.05V$	21.137
WE 712-429 Si switching diode.	0.682	$\pm 0.05V$	22.458
AA-442 Ge Schottky diode	0.281	$\pm 0.05V$	9.677
1N4148 Si diode	0.615	$\pm 0.05V$	9.308

The ideal diode model has no offset, and no series resistance. It is vertical at  $V_D=0V$ . The AA-442 Ge Schottky diode is the closest to the ideal diode model. It has the smallest  $V_t$ , so it has the lowest offset, and so its linear portion is closest to the y-axis. It also has a very small  $R_d$  of 9.677 Ohms. The 1N4148 Si diode is also very close to the ideal diode model. It has the smallest  $R_d$  of 9.308 Ohms and a fairly small offset, with a  $V_t$  of 0.615V. Visual inspection of the plotted I-V curves also supports these diodes' similarities to the ideal diode model. They are the closest to vertical of all the plotted diode I-V curves.

In general, the "warm" color LEDs (red, yellow) have lower  $V_t$  and also lower  $R_d$  compared to the "cool" color LEDs (blue, green, white). The warm color LEDs have  $V_t$  from about 1.9V to 1.7V, and  $R_d$  from about 9.5 Ohms to 21 Ohms. The cool color LEDs have  $V_t$  from about 2.4V to 2.65V and  $R_d$  from about 30 Ohms to 51 Ohms. There are some exceptions - the green LED is included in the "warm" color range - but otherwise, the colors with longer wavelengths have lower  $V_t$  and  $R_d$  than the colors with shorter wavelengths.