

LAB 2 - POWER AND EQUIVALENT RESISTANCE**Exercises:**

1) Preliminary calculations:

- a) Assuming you are using a $\frac{1}{6}$ W resistor from the resistor bins in McC305, what is the smallest resistance you could attach across a 5V power supply without exceeding its power rating? How much current would that resistor draw?
(Answers in terms of R)

$$\begin{aligned} \text{1/6 W resistor} \quad P &= IV = I^2 R = V^2 / R \\ \text{5V power supply} \quad I &= \frac{25}{R} \Rightarrow R = 150 \Omega \\ \text{assume Ohmic resistor} \quad I &= V/R = 5/R \text{ amps} \end{aligned}$$


- b) Find the maximum current and voltage for the following higher power resistor available in the larger resistor bins:
- 0.5W 30Ω
 - 1.0W 15Ω
 - 2.0W 36Ω

$$\begin{aligned} \text{b) 0.5 W, } 30 \Omega \quad P &= I^2 R \Rightarrow 0.5 = I^2(30) \Rightarrow I = 0.13 \text{ amps} \\ &0.5 = V^2 / 30 \Omega \Rightarrow V = 3.9 \text{ V} \\ \text{1.0 W, } 15 \Omega \quad P &= I^2 R \Rightarrow I = \sqrt{1}(15) \Rightarrow I = 0.26 \text{ amps} \\ &1.0 = V^2 / 15 \Omega \Rightarrow V = 3.9 \text{ V} \\ \text{2.0 W, } 36 \Omega \quad P &= I^2 R \Rightarrow I = \sqrt{2}(36) \Rightarrow 0.24 \text{ amps} \\ &2.0 = V^2 / 36 \Omega \Rightarrow V = 8.5 \text{ V} \end{aligned}$$


- 2) Design and build a simple circuit with a power source and a resistor, in which
- you do not exceed the current rating of a $\frac{1}{8}W$ resistor. You should use the 5V wall plug power supply, and any $\frac{1}{8}W$ resistor that you deem appropriate for this experiment. Observe/feel the temperature of the resistor by pressing your finger against the resistor.

Figure 1 (Left). Diagram of circuit not intended to exceed $\frac{1}{8}W$ current rating.

Figure 2 (Right). Circuit built not to exceed $\frac{1}{8}W$ current rating.

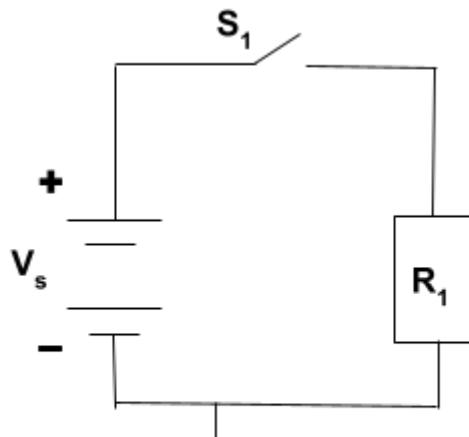
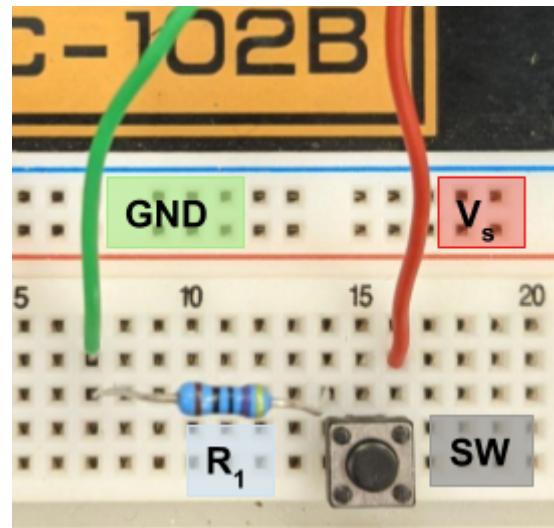
$$V_s = +5V \text{ DC}; R_1 = 470\Omega$$




To avoid exceeding the current rating of a $\frac{1}{8}W$ resistor, a resistor of 150Ω or greater should be used. In the circuit pictured above, a 470Ω resistor was used. Prior to circuit construction, the actual resistance was measured as 468Ω using a DMM. This is within tolerance.

The temperature of the resistor did not change when it was added to the circuit. It remained a similar temperature to the ambient temperature of the room.


- b) you expect to exceed the current rating of a $\frac{1}{2}$ W resistor. Observe/feel the temperature of the resistor by pressing your finger against the resistor.

Figure 3 (Left). Diagram of circuit intended to exceed $\frac{1}{6}W$ current rating.

Figure 4 (Right). Circuit built to exceed $\frac{1}{6}W$ current rating.

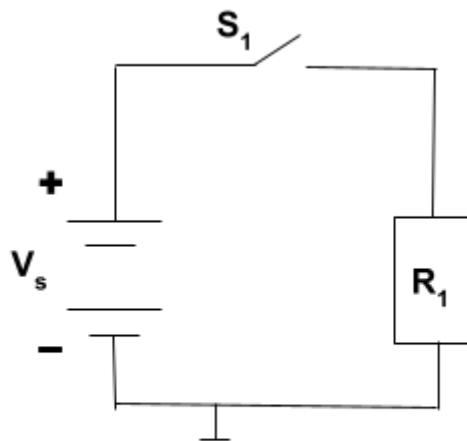

$$V_s = +5V \text{ DC}; R_1 = 75\Omega$$

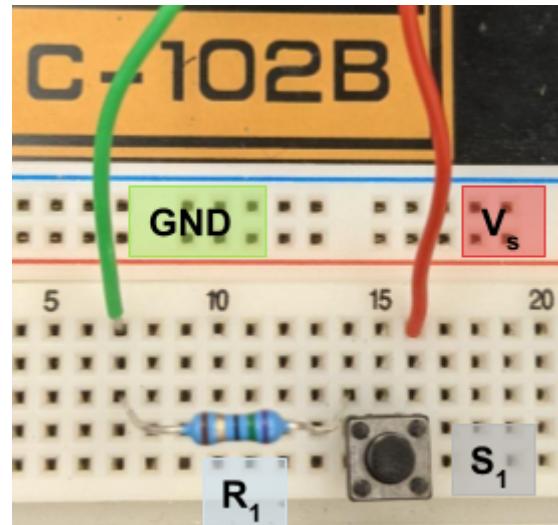


To exceed the current rating of a $\frac{1}{8}$ W resistor, a resistor of less than 150Ω should be used. In the circuit pictured above, a 75Ω resistor was used. Prior to circuit construction, the actual resistance was measured as 74.7Ω using a DMM. This is within tolerance.

The temperature of the resistor noticeably increased when it was added to the circuit. It was warm to the touch, and continued getting warmer the longer the circuit remained powered.

- c) Summarize what you observed including photos if anything interesting happened. Then explain why you think whatever you observed happened.

I observed that exceeding the current rating of the resistor caused it to dramatically increase in temperature. I think this is because more current means more electric power that is dissipated as heat by the resistor.

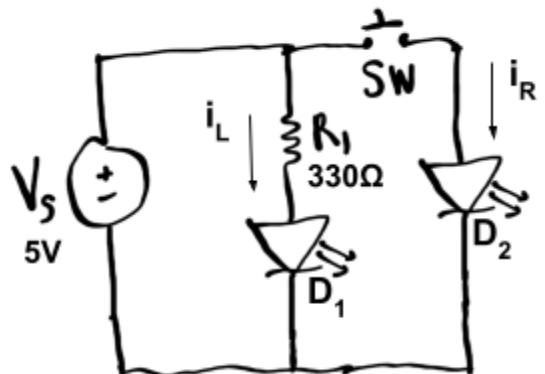
- 3) Build the circuit shown using a 5V power supply, and $R_1 = 330\Omega$. You can pick any color LED, but use the same color in each branch of the circuit. Measure the current in each branch, and observe the temperature of the two LEDs with the IR



thermometer. Note: the item labeled SW in the circuit is a button switch. Be sure the button is pressed when you are measuring the current in the rightmost branch of the circuit.

- a) Summarize what you observed including photos or video if anything interesting happened. Be sure you include any noticeable differences in current, brightness and temperature. Then explain why you think whatever you observed happened. Specifically address the role of the 330Ω resistor, since that item's presence/absence is the main difference between the two branches of the circuit.

Figure 5. Circuit built with two LEDs, a switch, and a 330Ω resistor.

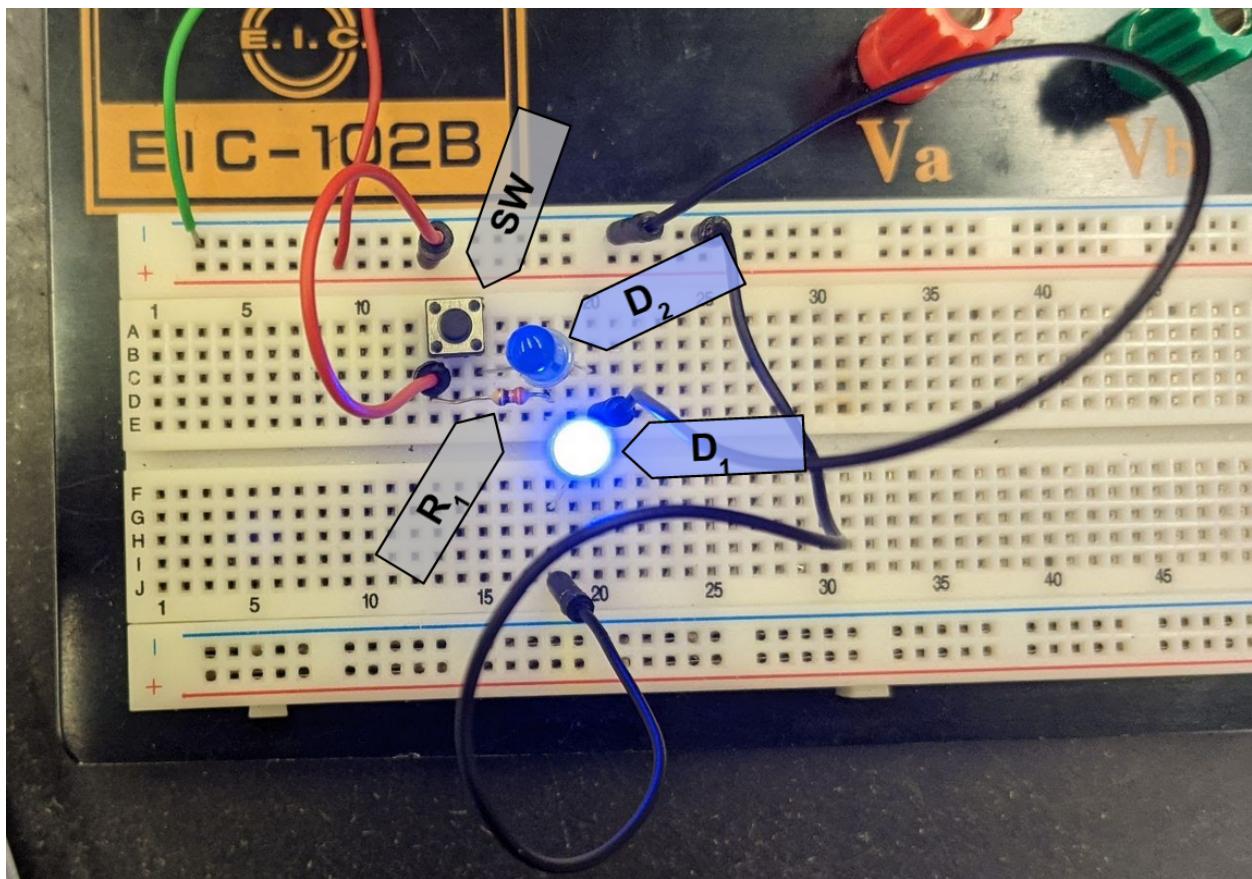

When the button switch was not pressed, LED D₁ was on steadily, while LED D₂ remained off, as it did not have any current flowing through it. When the button was pressed, D₂ was connected to the circuit and both LEDs were on steadily. A video of the circuit in both states is available here: <https://youtu.be/yGM0efh-o2Y>


LED D₁ was noticeably dimmer than LED D₂. The presence of the 330Ω resistor in series with D₁ meant that less current flowed through D₁ than D₂. Current i_L through the left branch of the circuit (containing the resistor and D₁) was measured with the DMM to be about 6.0-6.5 amps. A video of this measurement is available here: <https://youtu.be/NjVZlxHvjJk>

In contrast, current i_R through the right branch of the circuit (connected via button switch and containing only D_2) was measured with the DMM to be about 60-70 amps. A video of this measurement is available here: <https://youtu.be/2V4nRmUJsN8>

- b) Replace the 5V power source in your circuit with a 3V battery pack, and report the results as in part (a)

Upon replacing the 5V power source with a 3V battery pack, the circuit no longer appeared to function. Neither LED lit up, despite voltage measurements with the DMM confirming that there were no issues supplying 3V to the circuit. It turns out that the threshold voltage (measured with the LCR) for the blue LEDs used in the circuit is just below 3V. So the LEDs were only just barely receiving enough power for current to flow through the LEDs, meaning any changes in LED brightness were not dramatic enough to be easily seen.



Figure 6. Measuring the threshold voltage of an LED used in the previous circuit.

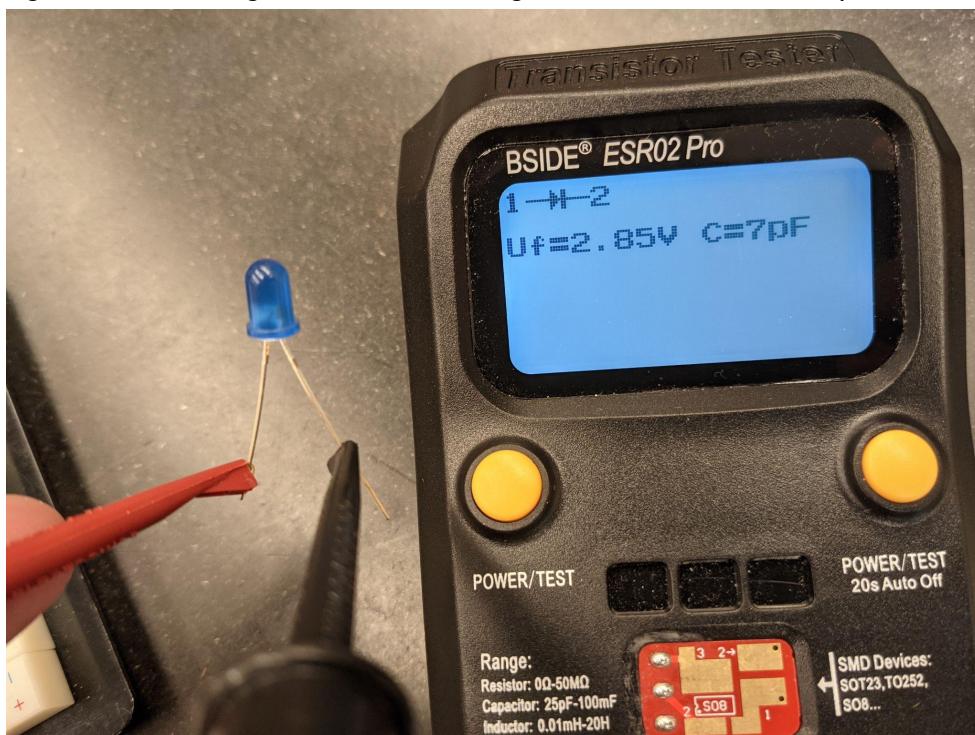



The blue LEDs were swapped out with yellow LEDs (measured to have a threshold voltage of approximately 2V), and the qualitative behavior of the circuit was the same as it was when powered by the 5V source.

- 4) Find the equivalent circuit resistance for each case drawn below. Your answer will be in terms of R . Show your work. Check your final answer against the posted solutions or by building the circuit and measuring the equivalent resistance with your DMM.

Circuit 1:

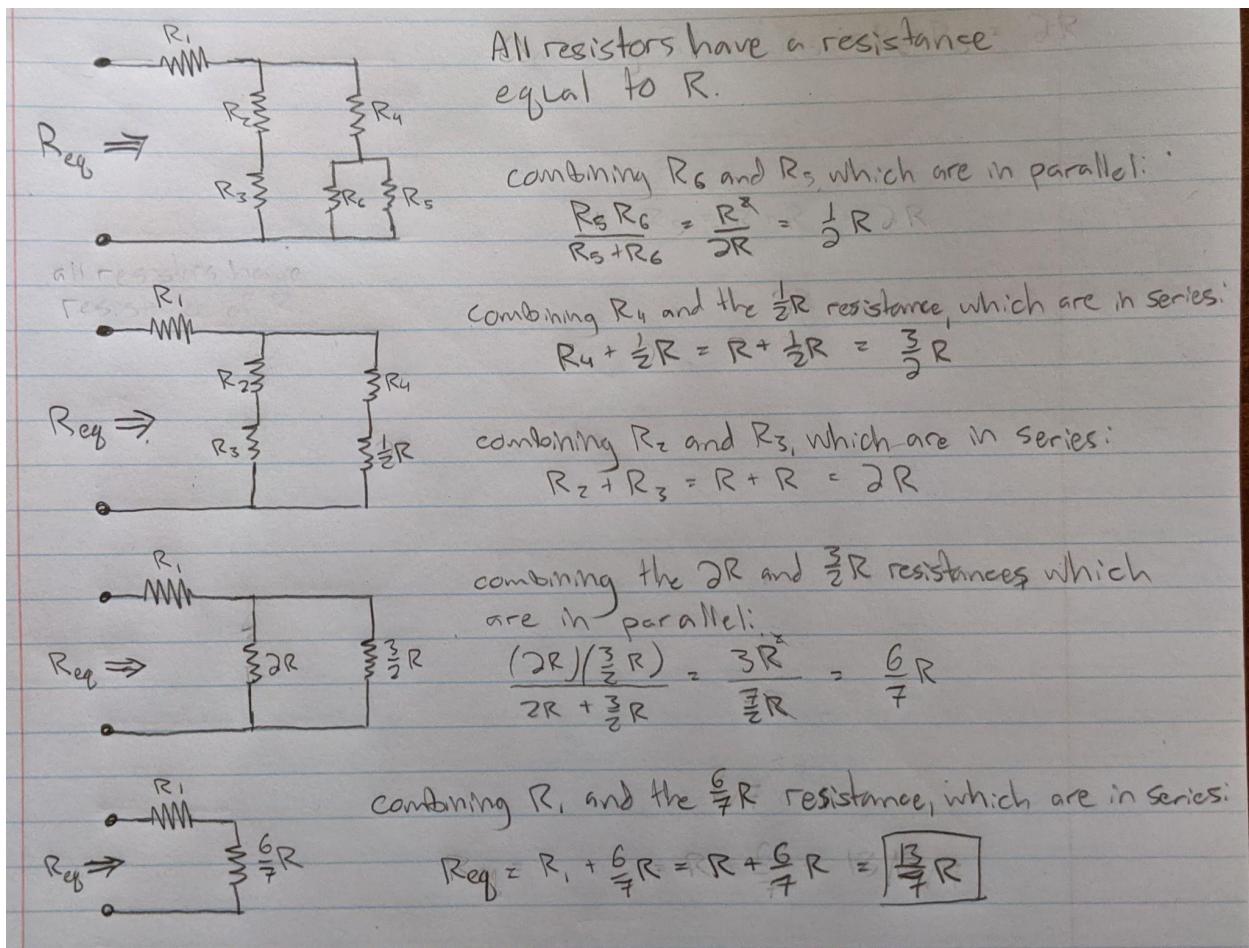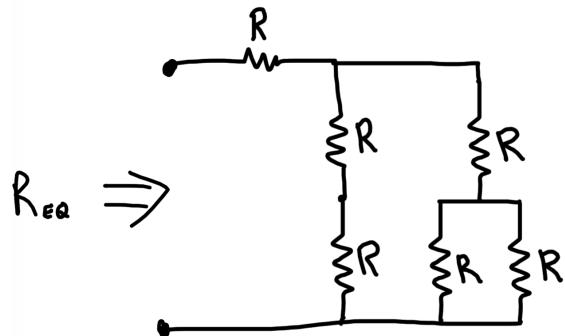

Circuit 2

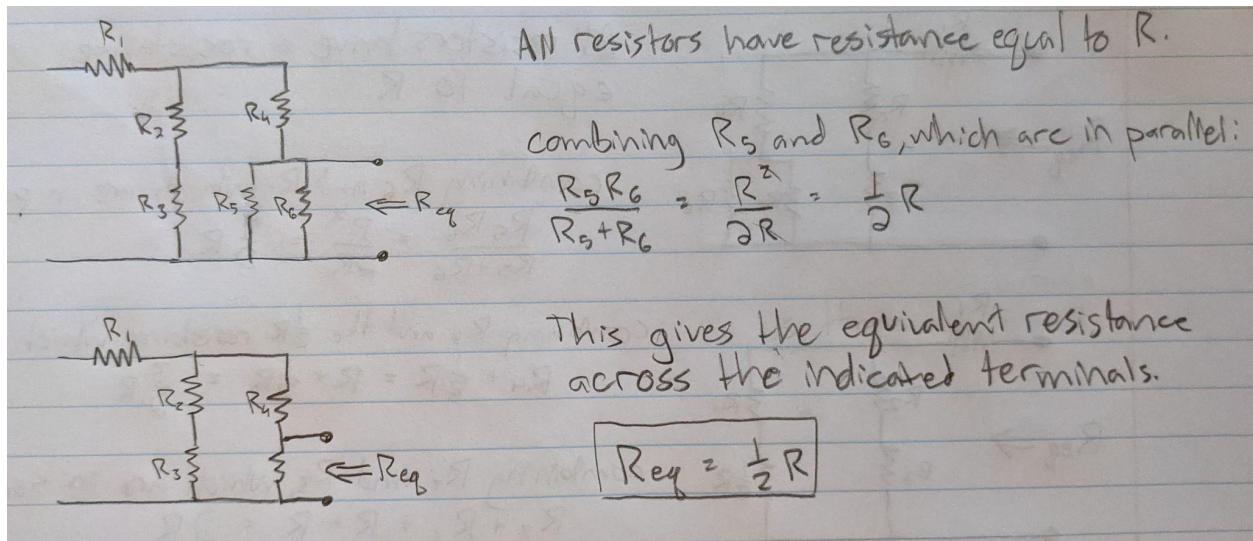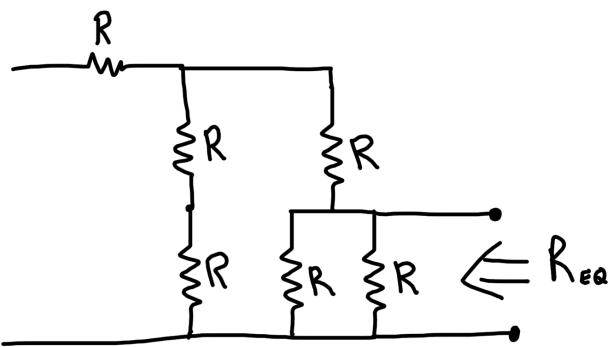

Circuit 3

